

# INDEX

## A

- A/D converter 104-105
- Accuracy 1, 2, 10, 13, 15-16, 18, 20, 22, 24, 42, 103, 105, 108, 112, 117, 119, 121-125, 129, 131, 134, 139, 143, 146, 161-163, 165, 167-168, 171-172, 177-179, 187, 202-203, 213, 221, 224-226, 245, 249, 266, 276, 292, 296-298, 304, 307, 309, 323-325, 327-328, 336, 347, 350-352, 358, 360, 364-365, 370, 372, 374-375, 378, 380-382, 385, 391, 393-394, 396-398, 465, 483, 485, 487-493, 501, 503-504, 506-508, 510, 512, 516, 521, 530, 533, 535, 540-550, 552-555, 561, 566
- See also* Percent registration
  - D/A converter 105-106
  - definition 7
  - demand 214-215
  - digital display resolution 106
  - factors of 161
  - guaranteed 554
  - importance of harmonics on 247-248
  - of instrument transformers 342-346, 380
  - over temperature 392-393
  - permanence of 302, 313
  - precision 552, 554
  - rating of instruments 124
  - ratios 552
  - voltage transformer 340-342
- Adjustments of a watt-hour meter 157-160, 176-177, 503-506
- Admittance, abnormal, testing for 374-375
- Alternating-current circuits 58-77, 78-85
  - capacitance in 65-67
  - capacitive reactance in 67-68, 70
  - formulas for 73
  - frequency in 59, 65, 67
  - impedance in 81
  - inductance in 63-65
  - inductive reactance in 65
  - Ohm's Law for 46-47
  - power factor of 60
  - power in 56, 76
  - sine waves in 27-28, 58, 60
  - single-phase series, formulas for 73
  - transformer connections for 85-88
  - transformers in 75-77
- Ammeter 7, 32, 43, 103, 111-113, 115, 117-119, 124, 204, 220, 264, 363-364, 366, 368-370, 374, 393-394
  - clamp volt 108-109
  - definition 7
  - electrodynamometer type 112-116
  - moving-iron type 111-112
  - permanent-magnet, moving-coil type 107-109
  - rectifier type 108
  - thermocouple type 108
- Ampere-Hour, definition 7
- Ampere-Turn, definition 7
- Analog-to-Digital Converter 104, 186-189
- Angles. *See* Trigonometry. *See also*
  - Phase angle
- Anti-creep holes 166, 506
- Artificial load. *See* Phantom load
- ASE cable 21
- "As found" test 334, 510-511, 516-517, 522
- "as left" test 334, 512-513, 517, 522
- Atom, structure of 89-90
- Automatic Meter Reading 7, 566-569
  - definition 7
  - electronic meter reading 565-566
    - handheld data entry terminals 565-566
    - handheld terminals, automatic data entry 566
  - Network Meter Reading 567-569
    - power line system 569
    - radio system 567
    - Telephone Dial-In System 569
    - Telephone Dial-Out System 568
  - retrieval of data 565
- Autotransformer 7, 233-235, 239, 348
  - definition 7
  - phase shifting 233-235, 239, 244

## B

Balanced circuits 78-83  
 Balanced load 115, 135, 137, 141, 173, 333, 338, 358, 454, 467-468  
 Balanced load, definition 8  
 Bar X, definition 22  
 Bearings in watthour meters 168-169, 523  
 Binary digital logic 98-100  
 Block-Interval Demand Meter 11  
   definition 11  
 Blondel's Theorem 3, 129, 132, 134, 138-139, 143, 145-146  
   application of 131-132  
   definition 8  
 Braking magnets. *See* Permanent magnets  
 Bridges, definition 8  
   Kelvin 8  
   Wheatstone 8  
 Btu, definition 8  
 Burden, calculation of 8, 111-112, 235, 273-274, 290, 292-293, 295-303, 305-308, 310-311, 324, 327, 339, 343-344, 346-347, 349-352, 354, 357, 360, 364, 369-370, 373-376, 378-379  
   calculation of 339-342  
   definition 8  
   effect on instrument transformer ratio and phase angle 297, 310  
   methods of expressing 340  
     polyphase 301, 340  
     secondary 292  
   standard 345, 351

## C

Calibrating constant 513-514  
 Calibration 2, 27, 125, 146, 160, 171, 173, 175-177, 185, 253-254, 259, 262-266, 331, 357, 373-374, 378, 392, 396-398, 488, 497, 499-500, 506, 512-513, 535, 541, 543, 549, 551-555. *See* Watthour meters, testing of  
   definition 8  
 Capacitance 3, 65-67, 380, 382, 390, 459  
   definition 8  
   in AC circuits 65  
 Capacitive reactance 8, 67-68, 70  
   definition 8  
 Chain of standardization 550, 552  
 Charts, for recorders 565  
 Circuit breaker 4, 53, 290, 350, 383, 457, 485  
   definition 9  
   fuses and 457

Circuit, balanced 78  
 Circuits 3, 25, 31, 40, 45-48, 50-51, 54, 56, 58, 63, 67-68, 72-73, 75, 83, 85, 88, 96, 98-102, 104, 109-110, 114, 119, 123-124, 129-132, 139-140, 148, 150, 165, 171, 175, 177, 181, 183, 186-187, 200, 202-203, 206-210, 212, 223, 230, 233, 237, 240, 244, 247, 253-254, 257, 273-277, 279-282, 289-290, 315, 346-347, 349-351, 353, 355, 357, 360, 363, 365-366, 368, 374, 378, 380, 402, 455-458, 463-464, 467-468, 480, 483, 485-486, 493, 495-496, 499, 506-507, 512, 517, 519, 523, 553, 555. *See also* Alternating current circuits  
   distribution 85  
   parallel 53  
   polyphase. *See* Polyphase  
   protection of 456  
   series 51  
   series-parallel 54  
   single-phase 73  
   three-phase 78. *See also* Polyphase  
   three-wire 9, 56  
   two-wire 9  
   wye. *See* Polyphase, wye connections  
 Circular mil 9, 47, 151  
   application of 46  
   definition 9  
 Clamp volt-ammeter 108-109  
 Clockwise, rotation 9  
 Clutch, demand meters 530-531  
 Compensating metering. *See* Transformer compensation for losses  
 Compensation of meters, overload 161-166  
   polyphase 172  
   temperature 165-166  
   voltage 164-165  
 Compensator, loss 16, 254-255, 264-266  
   definition 16  
 Complex numbers, calculations 34-36  
 Complex numbers, polar form 36-44  
 Complex Numbers, rectangular form 34  
 Conductor, grounding 13  
   definition 13  
   entrance, definition 21  
 Connected Load 9, 82-83, 139, 148  
   definition 9  
 Connection errors 461-465  
 Constants, calibrating 513-514  
   definition 9  
   dial 9  
   kilowatt 278-279  
   kilowatthour 278-279  
   register. *See* Register constant  
   watthour. *See* Watthour constant

- Copper losses 219, 250, 252, 259, 265-268
- Core losses 10, 220, 250-251, 269, 396  
definition 10
- Correction factor 15, 40-41, 123, 238-239, 295-296, 300, 307, 313-338, 342, 346, 354, 370, 377, 519  
definition 15
- Counters, photoelectric 506-507
- Creep or creeping 10, 166, 350, 485, 500, 503, 506, 511-512, 516-518, 523, 526  
definition 10
- Cumulative demand register 533, 563
- Current, alternating, *See* Alternating current
- Current, electron 91, 93  
hole 91  
induced, definition 14  
lagging, definition 16  
leading, definition 16  
measurement of 111, 113-115
- Curve drawing meter, *See* Recording
- Customer's high-bill inquiries 483-485
- Customer's load 254-255, 267-268, 270, 331, 336, 459, 464, 467-468, 473, 486, 493, 516, 520
- Customer's premises 2-3, 454, 458, 481, 487, 493-494  
testing on 514-521
- Cutout 10  
definition 10
- Cycle 10, 59-60, 62, 64, 73, 101, 153, 156-157, 183, 186-187, 197, 209, 224, 231, 374, 393, 396, 533, 557  
definition 10
- ## D
- d'Arsonval 112
- D/A converter 105
- Damping of an Instrument 10  
definition 10
- Damping, current magnet  
*See* Permanent magnets
- Dead-Front 11  
definition 11
- Delta Service 134, 136, 145, 147, 228-229, 454, 456, 482, 505, *See also* Polyphase, delta
- Demand meter, maintenance of,  
*See* Demand meter, testing of
- Demand Meter 11, 116-117, 179, 191-217, 279, 282, 285-286, 487, 529-530, 534, 536, 538-539  
ampere 116-117, 202-203  
application of 202  
classes of 195  
cumulative type 198, 200-201, 212, 239, 285, 533  
definition 11  
indicating type 198-200  
integrating 195-196  
lagged 12, 196  
mechanical 198, 215  
pulse storage 209  
pulse-operated 203  
  electronic type 203  
  indicating type 203  
  paper-tape 204  
  recording type 204  
  solid-state 207-210  
registers for 201-202, 211-217, *See also* Registers, demand meters for  
thermal operated 196, 204-206  
timing motor for 531-532
- Demand Meter, testing of 538-539  
advancing mechanism 530, 535  
clutch 530-531  
cumulative register 533  
maximum demand pointer 532  
mechanical registers 529-534  
procedures 533-536  
pulse-operated 538  
recording type 538  
resetting mechanism 531, 535  
timing motor 531-532
- Demand register, *See* Demand meter, registers for
- Demand scales 562-563
- Demand, constant 11, 538  
definition 11  
explanation of 191  
factor, definition 11  
interval 179, 191-193, 195-198, 200-204, 209-212, 215, 224, 227, 278-279, 281-282, 287, 530-537  
kilovar 202-203  
kilovoltampere 202-203  
maximum, definition 11
- Demand, pulse counting meters 282
- Detent 12, 230, 288  
definition 12
- Dial Constant 9, 560  
definition 9
- Digital display 24, 106, 377, 491, 506, 534-535, 537, 561, 565
- Digital electronics 89, 96-102
- Digital instrument 103-107, 122-123
- Digital multiplier 186-190, 246
- Direct-current circuits 45-46, 63  
formulas for 57-58  
Kirchoff's Law for application of 47-51  
Ohm's law for application of 46-47

resistance connected in,  
 network 51  
 parallel 53-54  
 series 51-52  
 series-parallel 54-56  
 three-wire Edison distribution  
 system 56-57  
 Disk, *See* Rotor  
 Distribution circuits 85-88  
 Diversity 12, 469  
 definition 12  
 Driving torque in a watthour meter  
 172-173  
 Dynamometers, *See* Electrodyamometer

## E

Eddy currents 12, 68, 153-158, 161,  
 166-167, 174-175, 220, 250  
 definition 12  
 Edison three-wire system 56  
 Effective resistance 12, 165, 290  
 definition 12  
 Effective value 12, 60  
 definition 12  
 Electrical degree 12, 132  
 definition 12  
 Electrical service, *See* Service, electrical  
 Electrodynamometer 112, 114, *See also*  
 Instruments, electrodyamometers  
 Electromagnet 13, 151-152, 162, 164,  
 166, 170, 175-176, 203, 491, 502  
 definition 13  
 Electromotive Force 13, 46, 61, 152, 156  
 definition 13  
 Electronic digital instrument 103  
 Electronic instrument 104, 106, 122  
 Electronics, solid-state 89  
 Energy 13, 45, 56, 58, 64, 72-73, 75, 77, 83,  
 89-91, 102, 124, 127-129, 131, 134, 140,  
 143, 151, 157, 171, 174, 178-179, 183-185,  
 188, 190-198, 204, 208, 210-212, 217, 220,  
 223-230, 243, 245, 250-251, 272, 275, 277-  
 279, 283, 285, 287-289, 323, 457, 461, 463,  
 467, 479, 487-492, 496, 507, 513, 531, 535,  
 543-544, 566  
 definition 13  
 Equations, basic laws of 25  
 Equipment, service 21, 351, 454, 458,  
 460-461, 464, 478  
 definition 21

Errors 2, 106, 109, 117, 123, 129, 133-134,  
 139-140, 143, 146, 148, 150, 160, 164-  
 165, 167-168, 173-175, 202, 220, 224-  
 225, 249, 266, 274, 281, 293, 295-296,  
 301-302, 304, 307-310, 312-313, 315-  
 316, 323, 325-331, 333-336, 338, 344,  
 352, 356-357, 360-361, 363, 370, 375-  
 378, 380, 393, 395, 461, 463-464, 468,  
 489, 504-505, 507, 517, 519, 545, 548,  
 552-555, 560, 566, *See also* Percent error  
 random 553  
 systematic 553

## F

Farad 13, 66  
 definition 13  
 Farber method for determination of  
 voltage transformer accuracy 340-342  
 Field, Magnetic 13  
 definition 13  
 mobile 487, 508, 521-522  
 stray 13  
 test 516-519  
 First reduction, *See* Shaft reduction  
 Flux and flux density, *See* Magnetic energy  
 Formulas, *See* name of specific formula  
 such as; "direct current circuits"  
 Friction, causes of 523  
 Foucault curenets, *See* Eddy currents  
 Full-load adjustment of a watthour meter  
 158, 503, *See also* Adjustments  
 Functions, trigonometry, *See*  
 Trigonometry  
 Fuses 4, 122, 356-357, 457, 460-461,  
 468, 479-480, 485  
 time delay 457

## G

Galvanometer 13, 371, 373-374, 380  
 definition 13  
 Gang Test boards 527  
 Gear ratio 13, 43, 168, 213, 524-525,  
 533-534  
 checking 524-526  
 definition 13  
 formulas of 43-44  
 Gear reduction 43-44, 534  
 Graphic demand meter,  
*See* Recording demand meters

Ground 13, 120-121, 148, 150, 171, 220, 273, 292, 302, 347-348, 350, 355, 360-363, 374, 380, 382, 384-385, 388-391, 396, 399, 454, 456-461, 463, 465, 468-469, 481-482, 484-486, 515, 518, 523  
 definition 13  
 return circuit 13  
 tester for 121

Grounding, conductor 13, 354-355, 360  
 definition 13  
 electrode 13  
 identification of 459-460  
 of electric circuits 458-460

Grounds, checking for 485-486

## H

Hall-effect multiplication 181, 246

Harmonics 77-78, 150, 167-168, 188-189, 219-221, 223, 225-226, 228, 244-248, 310, 375, 394, 493, 496-497, 545

Heater, for thermal operated instruments 109-110, 116-117, 205-206, 223, 283, *See also* Demand meters, thermal operated

Henry 13, 63  
 definition 13

Hi-pot tests 365-366

High-bill inquiries 483-485

Hole current 91-92

Horsepower 14, 75  
 definition 14

Hot-Wire Instrument 14  
 definition 14

## I

Impedance 14, 68, 77, 80-82, 134, 150, 152, 250-251, 257, 261, 276, 290, 293, 295, 297-299, 302-303, 305-306, 308, 313, 339, 346, 366, 374, 380, 396  
 definition 14  
 in AC Circuits 68-72

Impulse, *See* Pulse

Inactive meters 479

Indicating demand meter 561-564  
*See also* Demand meters, indicating type

Induced current 14  
 definition 14

Induced voltage 63-65, 75, 154, 294, 305, 380

Inductance 14, 63-65, 181, 303, 339, 373  
 definition 14  
 mutual 14  
 self 14

Inductive 14, 32, 61, 64-65, 67, 74, 84-85, 116, 152, 159, 222, 227, 230, 250, 255, 264, 266, 276, 326, 374, 380  
 definition 14  
 load adjustment, *See* Adjustments  
 of a watthour meter  
 reactance 67-68, 70, 81, 339, 494  
 reactance 14, 65

Installations, meter, *See* Service, electrical

Instrument, torque, *See* Torque  
 of an instrument

Installation of watthour meters 453  
*See also* Service

Installations, meter 264, 479, 519, 567

Instrument transformers 112, 130, 139, 148, 150, 178, 189, 200, 289, 291-292, 304, 313, 315, 322-325, 327-332, 334-336, 340, 342, 344, 346-347  
 application of 324-338  
 basic theory of 291-313  
 burden capability of 350, 376, 389  
 burden on 112, 273, 303, 311  
 calculation of 339-342  
 definitions 8, 290  
 effect on ratio, phase angle 297-298  
 methods of expression 340  
 polyphase 340  
 secondary 112, 292, 296-297, 299, 301-303  
 standard 344, 351

calculation of meter accuracy  
 settings 327

compensating error of 323-324

connections of 353-361

correction factors for 313-317, 322-324  
 application of 324-337  
 final 322-323  
 phase angle 314-318, 320, 322, 328, 342, 346  
 tables of 318-321  
 ratio 295-296, 300, 307, 313-314, 323, 327-328, 334, 337, 346, 377  
 table of 314

current 302, 313, 315-317, 322-323, 325, 328, 330-332, 334, 336, 342-346, 348, 351-352, 362-369, 372-375, 378-380, 384, 386, 390, 392-393  
 actual 304, 308  
 burden on 339  
 connections of 351, 357  
 dangers due to open secondary  
 of 313  
 demagnetizing of 379  
 difficulties with low ampere-turn  
 designs of 311  
 effects of, burden on ratio and  
 phase angle of 308

- common secondary leads 311
- frequency on ratio and phase angle of 309
- primary current on ratio and phase angle of 308
- secondary leads on ratio and phase angle of 310
- waveform on ratio and phase angle of 310
- ideal 302
- marked ratio of 304
- permanence of accuracy 313
- phase angle of 307
- phasor diagram of 304
- polarity of 302
- ratio correction factor of 307
- secondary burden on 302
- true ratio of 304, 307
- turn ratio of 304
- testing of 365
  - AC hi-pot test 365
  - by comparative method 370
  - by compensated standard method 378
  - by deflection method 370
  - by direct method 370
  - by Knopp comparator 376-380
  - by Leeds and Northrup test set 371, 373
  - by null method 370
  - for adequate insulation of 365
  - for shorted term 369
  - to check polarity of 366
  - to determine ratio and phase angle of 369
- type, bar 349, 351
  - bushing 350
  - double ratio 349
  - miniature 350
  - multi-core 349
  - split-core 349
  - three-wire 348-349
  - window 349
  - wound 348
- verification of connections of 361
- voltage 24, 148, 150, 206, 235, 251, 257-258, 264, 288, 291, 293, 296, 299, 302
  - actual 293, 295
  - burden of 292
  - connections of 353
  - definition 24
  - effects of burden on ratio and phase angle of 297
    - common secondary leads on ratio and phase angle of 301
    - frequency on ratio and phase angle of 298
    - primary voltage on ratio and phase angle of 297
    - secondary leads on ratio and phase angle of 299
    - temperature on ratio and phase angle of 298
    - waveform on ratio and phase angle of 298
  - ideal 291
  - marked ratio of 292
  - phase angle of 296-297
  - phasor diagram of 293-295
  - polarity of 292
  - ratio correction factor of 295
  - selection of 350
  - true ratio of 292, 295
  - turn ratio of 292
- Instruments, indicating 3, 42, 103, 369-370, 496, 522
  - accuracy rating of 124, 552
  - ammeter, *See* Ammeter
  - care of 122
  - clamp volt-ammeters 108-109
  - current transformer field test set 111-112
  - effect of mechanical defect on 123
  - electrodynamometers 112
    - applications of 113
  - influence on circuits of 124
  - Lincoln ampere demand meter 116
  - maintenance on 125
  - mechanical effects 123
  - megger 120-121
  - moving-iron type 110
    - application of 111
  - ohmmeters 119
  - permanent-magnet, moving-coil type 107
    - applications of 111-112
  - precision of 552
  - readability and resolution of 554
  - rectifier type 108
  - scales of 117
  - selection of 121
  - stray fields, influence on 123
  - temperature, influence on 123
  - thermal ampere demand meters 116-117
  - thermocouple type 109-110
  - voltmeter, *See* Voltmeter
  - wattmeter, *See* Wattmeter
- Insulation tester, megger 120
- Integrating demand meter 196
- Interference 4, 172-174, 480
- Interval, demand 179, 191-193, 195-198, 200-204, 209-212, 215, 224, 227, 278-279, 281-282, 287, 530-537

## J

Joule, law of 15, 56, 58, 500  
definition 15

## K

Kelvin bridge 8  
description 8  
Kilo 15  
description 15  
Kilovarhour, *See* Varhour  
Kilovar and kilovoltampere metering  
219-220, 222, 225, 228, 244  
autotransformers for 233  
cross phasing method of 236  
of four-wire, three-phase circuits 235  
of three-wire, three phase 234  
phase relations for 222, 241  
phase sequence 230  
special meters for 239  
theory of 220  
Kilovar demand 202  
Kilovoltampere demand 202-203, 561,  
*See* Voltamperehour  
Kilowatt, *See* Watt  
Kilowatthour, constant 278-279  
Kilowatthour meters, *See* Watthour meter  
Kirchhoff's Laws 47-51, 135, 467  
application of 47-51  
Knopp instrument transformer  
comparator 376-380  
KVA 15, 193-195, 219-224, 227-230, 250-  
251, 253, 257, 261-262, 268-270, 395  
definition 15  
metering of 225-226, *See also* Kilovar  
and Kilovoltampere metering

## L

Laboratory, the meter  
*See* Meter Laboratory  
Lag adjustments 159-160, 503-504, 513  
Lagged demand meters 195-196, *See also*  
Demand meters, thermal operated  
Lagging current 16, 67, 317, 512  
definition 16  
Laminated core 16  
definition 16  
Leading current 16, 67  
definition 16  
Leeds and Northrup test set 371-374

Lenz's Law 16, 63  
definition 16  
Light emitting diode 16, 104, 507, 509-510  
definition 16  
Light-load adjustment 158, 164, 166,  
176-177, 254, 264, 503, 506, 513  
Lightning arrester 120, 351, 456-457  
Lincoln ampere demand meter 116-117  
Liquid Crystal Display 16, 104, 209  
definition 16  
Load, artificial 16, *See also* Load, phantom  
balanced 8, 115, 135, 137, 141, 173,  
333, 338, 358, 454-455, 467-468  
compensation 16  
overload 161-164  
definition 16  
factor 16  
phantom 18, 331, 336, 493-495,  
516-517, 519  
resistance 496  
system 16  
water heater 283-285, 287, 468, 484  
Loading transformer 16, 374, 494-495  
definition 16  
Location of meters 251-252  
Locked-out meters 479  
Loss compensation 16, 250-251, 253,  
255, 257, 261-262, 267, 272, *See also*  
Transformer, compensation for losses  
definition 16  
Losses core 10, 220, 250, 269, 396  
definition 10  
transformer, *See* Transformer,  
compensation for losses

## M

Magnet, brake 151, 157, 168, 172, 176, 264,  
506, 513, *See also* Permanent magnets  
damping, *See* Permanent magnets  
permanent, *See* Permanent magnets  
retarding, *See* Permanent magnets  
Magnetic 13, 58, 63, 68, 73, 75-77, 129,  
153-154, 158, 162, 164-165, 168, 523  
field 13, 64, 75, 110, 112, 115, 152-153,  
156-157, 181-182, 185, 220, 250,  
386-389, 492  
flux 128-130, 153, 158, 181, 290, 362, 523  
Magnetism 110  
Magnetomotive force 16  
definition 16  
Maintenance of, demand meters, *See*  
Demand meter, testing of, instruments  
watthour meters, *See* Watthour meter,  
maintenance of

- Marked ratio of instrument transformers  
15, 292-293, 296, 302, 304, 307, 313,  
323, 349, 368-369, 386, 389  
definition 15
- Mathematics 25-44
- Maximum average power 194
- Maximum demand 191-198, 200, 213, 254,  
272, 285, 529, 530, 533, 536, 561-563  
explanation of 194  
meters, *See* Demand meters  
pointer 532
- Measurement of 111  
AC current 111, 113-115, 364  
AC voltage 103, 112, 115  
demand, *See* Demand meters  
frequency 116  
power 113  
power factor 115  
resistance 118-120  
speed 506  
varhours 230  
VARs 230  
watthours, *See* Watthour meters
- Mega 16  
definition 16
- Megger ground tester 121
- Megger insulation tester 120
- Memory circuits 100-102
- Metal-clad switchgear 480
- Meter accuracy, *See* Accuracy
- Meter bearing, *See* Bearings
- Meter, demand, *See* Demand meters
- Meter department 1-6  
duties 1-2
- Meter installation 254-255, 266, 474-478,  
482, 518
- Meter laboratory 117, 123, 130, 175,  
488, 541-555  
accuracy ratios for 552  
accuracy vs. precision in 552  
accuracy, guaranteed of 554  
chain of standardization 550-551  
chart of 551  
cross checking between laboratories  
554  
functions of 553  
fundamental standards in 543-548  
cells, standard 543  
primary watthour 547  
resistors 543  
secondary watthour 545  
time 543  
watt 544-545  
working watthour 548  
location of 554-555  
operation of 555  
random errors of 553  
scope of 541-542  
systematic errors of 553
- Meter, location of 251-252, 468-469, 515
- Meter personnel 2-7  
computations used by 40-44  
customer contacts 2-3  
good practices for 481-483  
knowledge required by 3-4  
opportunities for 2  
safety practices by 5-6
- Meter, reading of 2, 179, 192, 273, 522,  
557-569  
demand meters 561-565  
constants, registers used in 560-561  
indicating 561-564  
recording 538  
reset 562-564  
sealing of 564  
watthour 558-560
- Meter sequence 17, 460  
definition 17
- Meter sockets 363, 458, 469-475  
adaptors for 475-476
- Meter testing, *See* Demand meter, testing  
of; Watthour meter, testing of
- Meter watthour, *See* Watthour meters
- Meter, selection of 121-122, 469
- Metering computations 40
- Metering off-peak water heater loads  
283-284
- Micro 17  
definition 17
- Microprocessor 89, 102, 181, 187, 214,  
246, 257, 534-536, 565
- Mil 17  
definition 17
- Milli 17  
definition 17
- Motor, timing 531-533, 538
- Multi-stator VARhour meters  
*See* Watthour meters, multi-stator
- Mutual inductance, *See* Inductance,  
mutual

## N

- National Electrical Code 17, 453-454,  
458, 460  
definition 17
- National Institute of Standards and  
Technology (NIST) 2, 370, 541
- Network 134  
meters for 132, 134, 521  
service 132, 134, 454-455

Neutral wire 145, 361, 458, 467, 485  
 Null method 370, 376-377  
 Number systems 96, 98, 100  
   binary 96  
   decimal 96  
   hexadecimal 97

## O

Off-peak load, metering of 283  
 Ohm 17, 53, 120, 124, 300, 305, 311, 357,  
 374, 542-543, 550  
   definition 17  
 Ohm's Law 18, 25, 46, 50-57, 67, 73, 83, 118  
   application of 46-47  
   definition 18  
   statement of 25  
 Ohmmeters 119-120  
 Optical port 18, 281, 565-566  
   definition 18  
 Optical probe 18, 540, 565-566  
   definition 18  
 Outdoor installations 478  
 Overload compensation 157, 161, 168, 174

## P

Parallel circuit 26, 51, 53, 72  
 Parallel-series circuit 51, 54-56  
 Paralleling current transformer  
   primaries 274  
 Paralleling current-transformer  
   secondaries 273  
 Peak load 18  
   definition 18  
 Percent error 18, 40-43, 325, 328, 331,  
 333-334, 336, 343, 517  
   calculations for instrument  
   transformers 328-329  
   definition 18  
 Percent registration 18, 40, 167, 256,  
 262, 266, 501-503, 517, 522  
   calculation of 40, 42-43, 326-329  
   definition 18  
   with instrument transformers 326  
 Permanent magnets 111, 158, 162, 171, 254  
   in moving-coil instruments 107  
 Phantom load 18, 331, 336, 493, 495-496,  
 516-517, 519  
   definition 18  
 Phase angle 18, 31-32, 39, 58-62, 74-75,  
 78, 84, 115, 128, 134, 137, 142, 167, 174,  
 181, 183, 223-224, 229-231, 243-244,  
 247, 266, 274, 297-300, 313-349, 356-357,  
 362-366, 369-380, 398, 487, 489, 493-495,  
 518, 544, 546, 548-549  
   of current transformer 307-310  
   of voltage transformer 296-301  
 Phase angle correction factor 314-317,  
 322, 328, 342, 346, 370  
   tables of 318-321  
 Phase shifter 18, 246, 371, 373-374, 380  
   definition 18  
 Phase shifting transformer,  
   *See* Autotransformers  
 Phase, rotation 231, 363-364, 482  
   indicators of 231  
   sequence 18, 134, 230-232, 246, 518  
   definition 18  
 Phase-displaced metering, application  
 229-230  
 Phasor 18, 68, 74, 80, 82, 84, 132, 140-141,  
 159, 222, 239, 241, 295, 518  
   definition 18  
   diagram, definition 18  
   examples of 60-63, 79, 135-136, 139,  
   141, 143, 146-148, 159, 231, 236,  
   293-297, 299-301, 304-307, 311,  
   315, 317, 323, 353-354, 357, 359,  
   361, 363-364, 454, 505, 518  
 Photoelectric tester or counter 18  
   definition 18  
   with rotary stepping switch 506-507  
 Polarity 19, 76, 93, 110, 112, 236-237,  
 281-282, 295-296, 306, 308, 340, 352-  
 353, 357, 360, 362-363, 366-368, 370, 380  
   definition 19  
   instrument transformers 292, 302  
 Pole-top metering 481  
 Polyphase 3, 129-131, 142, 146, 148, 171-  
 180, 187, 190, 200, 220, 230, 247, 265,  
 301, 311, 325, 328, 330, 332-334, 336,  
 353, 363, 454, 464, 504, 507, 510, 512  
   delta connection 228  
   wathour 131-132  
   wye-connected 340  
 Portable standard meter 24, 264, 268, 489,  
 541-542, 544-545, 547-548, 550, 554  
 Potentiometers 377  
 Potentia electrical, *See* Voltage  
 Power 19, 137, 139, 141-142, 146-147, 151,  
 156-157, 178, 180-196, 203, 206, 209-213,  
 217, 219-220, 223-230, 246, 248-249,  
 274-275, 281, 288, 298, 315, 323, 334,  
 336, 348, 370, 385, 388, 394-395, 454,  
 457, 461, 480, 482, 490, 493-494, 508,  
 520-522, 531, 535, 537, 555, 564, 569

definitions 19  
 in AC circuits 72-75, 83  
 in DC circuits 56  
 in polyphase circuits 129-133, 142, 174  
 measurement of 113, 115  
 triangle of 83-85, 194, 221, 223  
 Power factor 3, 19, 31-32, 60-61, 67, 70-75, 77, 84-85, 112-113, 115, 133, 136-137, 139-143, 152, 156-160, 165, 167, 175-177, 203, 206, 217, 219, 221-222, 229-230, 232, 234, 236-237, 239-240, 242-243, 247, 251, 257, 262, 265-268, 270, 290, 292, 295, 300, 303, 305, 311, 315, 317, 322, 324-326, 328, 330-336, 338-343, 346, 364, 370-371, 373, 394-395, 495, 505, 517-518, 544-546, 548  
   definitions of 19, 219  
   equations of 31-33  
   meters to measure 115  
 Precision vs. accuracy 552  
 Primary 1, 19, 75-76, 86, 111-112, 148, 185, 205, 226, 255, 270, 272-273, 275, 289, 291-298, 301-302, 304-317, 323, 326, 328, 334, 348-354, 356, 362-363, 365-366, 368, 373-374, 379-380, 384, 386, 388-396, 455, 469, 478-479, 493, 520, 525  
   definition 19, *See also*  
     Instrument transformers  
 Protection, circuit 456-457  
   fuses 457  
 Pulse 19, 104, 178, 180, 183-187, 190, 209-210, 212-215, 224-225, 275-279, 280-282, 489-491, 493, 499, 510, 536, 539-540  
   definition 19  
   operated demand registers 197, 203, 207-208, 538  
   totalization 275, 282-283

## Q

Quadrants 39, 243  
   measurements 243-244

## R

Random errors 552-553  
 Ratio correction factors,  
   *See* Instrument transformers,  
   ratio correction factors of  
 Ratio gear, *See* Gear ratio  
 Ratio, marked, *See* Instrument  
   transformers, current and voltage  
 Ratio, register, *See* Register ratio  
 Ratio, true, *See* Instrument transformers,  
   current and voltage  
 Ratio, turn, *See* Instrument transformers,  
   current and voltage  
 Ratios, accuracy 552  
 Reactance 20, 67, 69, 81, 159, 165, 167,  
   295, 298, 305, 494  
   definition 20  
 Reactiformer 20, 233  
   definition 20  
 Reactive power, *See* VARs  
 Reactive voltamperes 20, 222  
   definition 20, *See also* VARs  
 Reactor 20, 115, 231, 379  
   definition 20  
 Reading of meters, *See* Meter, reading of  
 Readability of instruments 374, 380  
 Recording demand meters 196-198, 200,  
   203-204, 211, 217, 529, 534, 538, 561,  
   565, 567  
 Rectifier 108-109, 168, 459, 555  
   instrument type 108  
 Reference standards 496, 541, 543, 552, 554  
 Register constant 20, 43-44, 254, 506, 511,  
   517, 520, 524-526, 560-561  
   checking 524-526  
   definition 9, 20  
   formulas of 43-44  
 Register ratio 3, 20, 168, 202, 254, 289,  
   485, 502, 511, 517, 520, 530, 533-534, 560  
   checking 524-526  
   definition 20  
   formulas for 43-44  
 Register, demand meters application of 202  
   cumulative type 200  
   electronic 211-217  
   mechanical 529-536  
   testing of 537  
 Register, watthour meter 198  
   formulas for 43  
   maintenance of 523-526  
   testing of 524-526  
   two-rate 283-284, 286, 560  
 Registration 2, 20, 129-130, 134, 146,  
   158-159, 164, 173, 175-176, 198, 203,  
   211, 237-238, 253-254, 262, 266-268  
   definition 20  
   percent, calculation of 40-43, 267-271  
   definition 18  
 Relay, auxiliary 281  
   totalizing 279-280  
 Resistance 20, 25-26, 46-47, 49, 51-53, 55-  
   57, 64, 66, 68, 70, 81, 103, 108, 111, 113,  
   115, 120, 124, 150, 158, 159-160, 165-167,  
   170-171, 182, 206, 222, 239, 246, 250, 257,  
   267, 270, 277, 293, 295, 298-303, 305, 311,  
   339, 346, 353-357, 360, 361, 363, 375, 379,  
   458-459, 462, 470, 481-482, 493-494, 503-  
   504, 523, 542-543, 550

- definition 20
  - in AC circuits 67-68
  - in DC circuits 46
  - load 496
  - measurement 118-120
  - Resolution 105-107, 186-188, 199, 203, 215, 224, 281, 490-491, 554
  - Rheostat 21, 371
    - definition 21
  - Right triangle 28-29, 31-32
  - Root-Mean-Square Value 12, 206
    - definition 12
  - Rotating standard, *See* Portable standard meters
  - Rotor (disk) 112, 129-130, 151-153, 157-158, 168-169, 175-176, 197-198, 200-201, 276-277, 524, 532
- S**
- Safety 2-3, 5, 183, 280, 352, 355, 360, 363, 365-366, 386, 453, 460, 474-475, 483, 490, 515-516, 519, 557, 564
  - Scales, instrument 117
  - Scientific notation 33
  - Scott connections 253
  - SE cable 21
    - definition 21
  - Secondary watt-hour standard winding 19
    - definition 19
  - Selection of instruments 121
    - meter capacity 469
  - Self inductance 14
    - definition 14
  - Semiconductor 77, 89, 91, 94-95
    - definition 91
    - diode 93
    - N type 92-93
    - P type 92-93
  - Series circuit, *See* Direct-current circuits
  - Series-parallel, *See* Direct-current circuits
  - Service 1-3, 21, 111, 121, 128-129, 131-134, 138-141, 143-144, 146-147, 171, 175-181, 183, 202, 220, 228-229, 235, 253, 257, 264, 266, 270, 272, 278, 283-284, 287, 348-349, 352, 357, 363, 365, 368, 374-375, 396-398, 453-487, 493, 497, 500, 502, 504, 510, 514-518, 521-523, 533, 535, 557, 566-567, 569
    - checking for grounds on 485-486
    - circuit protection of 456-458
      - grounding of 458-460
    - classes of 454-455
    - conductor identification by color 460
    - conductors 21
      - definition of 21
    - connection errors in 461-464
      - definition of 21
    - distinguishing between four-wire delta and four-wire wye 456
    - distinguishing between three-wire network and three-wire single-phase 455-456
    - drop 21, 453-454
      - definition of 21
    - entrance conductors 21, 454
      - definition of 21
    - equipment 21
      - definition of 21
    - good practices for metering personnel, installation 481-483
    - inactive and locked-out meters 479
    - installing 474-475, 480
      - in metal-clad switch gear 480
      - of bottom connected meters 476-478
      - of socket meters 475-476
        - with instrument transformers 478
    - investigation of customer high-bill inquiries 483-485
    - location of meters in 468-469
    - meter sequence for 460
    - meter sockets for 469-474
    - metering two-wire service with three-wire service 465-467
    - neutral wire of 467-468
    - outdoor installations of 469, 478
    - pole-top metering in 481
    - socket adaptors for 475-476
    - test switches for 479-480
  - Shaft reduction 21, 502, 520, 524-525
    - definition 21
  - Shop tests 18, 502, 507, 510-514, 518, 522, 534, 538, 548, *See also* Watt-hour meter, testing of
  - Short circuit 21, 75, 250, 303, 306, 357, 457, 471, 478, 485, 515, 521, 523, 526
    - definition 21
  - Silsbee current transformer set 372-375, 378-380
  - Sine waves 27-28, 58, 60, 62, 78, 168, 186, 220, 231, 497, 555
  - Single-phase 58, 72-74, 78, 83, 115, 128-129, 132, 134, 148, 154, 171-173, 176-178, 190, 221, 229-230, 267, 274, 283, 301, 323, 324, 331, 333-334, 336, 340, 348-349, 353-354, 357-358, 364, 373, 454-455, 458, 462-464, 467-468, 496-497, 505, 507, 514
  - Single-stator watt-hour meter 129-130, 134-135, 148, 151, 157, 161, 171-173, 266, 292, 302, 502, 504, 510

## Single-stator watthour meter tests

- 510-512
- Socket 21, 130-131, 170-171, 178, 210, 250, 363, 421, 456-458, 460, 465, 467, 469, 470-477, 479, 485, 516
  - adaptors for 475-476
  - definition 21
  - meters for 474-475
- Solid-state, electronics 89-102
  - demand recorders 207-210
  - metering 178-188, 190, 251, 257, 272, 278, 292, 348, 364, 474, 506-508, 510, 512-513, 568
  - watthour metering 181
- Special metering 134, 178, 192, 239, 249-288, 359, 475, 522
- Speed 77, 107, 129, 151, 157-158, 161-162, 166, 169, 172-173, 219, 253, 264, 271, 287, 333, 336, 386, 465, 503, 521, 526, 529, 533-534, 560
  - measurement of 506
- Spindle reduction, *See* Shaft reduction
- Standard burden 309, 343-345, 351, 374
- Standard cells 543
- Standard resistors 369, 541, 543
- Standards iii, 1-2, 4, 43, 47, 117, 168, 175, 183, 331, 333-334, 336-337, 352, 365, 370, 381, 386, 389-390, 398, 470, 488, 490-492, 507, 520, 526, 530, 534, 536-537, 540-555
  - fundamental 543, 547
  - portable 548, *See* Portable standard meters
  - potentiometer 550, 555
  - primary watthour 547
  - reference 488
  - rotating, *See* Portable standard meters
  - secondary watthour 545-546
  - time 543
- Standardization, *See* Meter Laboratory
  - See also* Standards, fundamental
- Stator 22, 112, 129-132, 134, 136-137, 140-143, 146-148, 151-153, 157, 171-177, 253-254, 256, 264-267, 270, 274-275, 288, 328, 334, 336-338, 359, 363-364, 504-506, 512-513, 519, 521
  - definition 22, *See also* Electromagnet
- Stray fields 122-123, 352, 374, 378, 523
- Systematic errors 552-554

## T

- Temperature 22, 94, 109, 116, 123, 161, 163, 166, 172, 182, 194, 196, 205-206, 223, 249, 298, 351, 388-390, 392-393, 469, 543, 553-554
  - compensation, definition 22, 161, 165-166
- Terms and definitions 7-24, 289-291
- Test switch 250, 266, 362, 364, 375, 435-436, 443, 479-480, 519, 521
- Test tables 494, 506, 548
- Testing, demand meters
  - See* Demand meters, testing of
  - on customer's premises 514-521
  - instrument transformers, *See* Instrument registers 215, 524-526, 533, 535-539
  - watthour meters, *See* Watthour meters, testing of
- Tests, field 121, 179, 365, 375, 506, 516, 518-519, 521-522, 534
  - interference 175
- Tests, shop 510-514, 518, 522, 534, 538-539, 548
- Theory of torque production 151-157
- Thermal ampere demand meter 116-117
- Thermal demand meters, *See* Demand meters, thermal operated
- Thermocouple 22, 109-110
  - definition 22
  - instrument 109, 110
- Thermoelectric Effect 22
  - definition 22
  - laws 23
- Three-phase watthour meters 129-146
- Three-strator watthour meter 138-148
- Three-wire system 23, 241, 279, 458
  - definition 23
  - solution of 56, 57
- Three-wire watthour meter 129, 148, 166
- Time, standard 543
  - switches 283-285
- Time-delay fuses 457
- Time-division multiplication 181, 183-185
- Time-of-use metering 23
  - definition 23
  - demand meters 197, 210-211, 213, 536
  - meter reading 565-569
- Timing, watthour meters 506
  - motor for 531-532
- Torque balance adjustment 176-177, 264, 504, 512
- Torque of an instrument 23, 107-108, 110-113, 115-116, 137
  - definition 23

of a watthour meter 146, 151-158, 162, 164, 166-167, 171-177, 239, 241-242, 264

Totalization 192, 273-275, 278-279, 281-283, 359

Totalizing relay 279-282

Transconductance multiplier 185-186

Transformer 23, 75

- calculation losses for 257-262
  - application of 257
  - methods of 259-260
- compensation for losses 249-251, 254
- compensator for 264-266
  - calibration of 264-266
- loss meter 263-264
  - calibration of 263-264
  - test of 264

Transformer, correction factor  
*See* Instrument transformers, correction factors for

Transformer, current, *See* Instrument transformers, current

Transformer ratio 23, 43, 267, 309, 314, 323, 326, 330

- definition 23

Transformer ratio, current 43, 261, 560

Transformer ratio, voltage 43, 261, 269-270

Transformer, phase-shifting 233, 240, 348

Transformer, power 249-250, 252, 258, 267, 290, 350, 480, 493, 521

- connections of 252-253
- definition 23
- loading, definition 16
- losses in 250-266

Trigonometric functions 29-33, 241

Trigonometry 31, 74, 85, 222

Trough, *See* Socket

Two-rate registers, *See* Registers, two-rate

Two-stator watthour meter 132-143, 146-148

Two-wire meter 128, 446

## U

Universal, meters 178, 403-405, 408-451

## V

VARhour 23, 32, 234, 237, 241-243, 257, 264, 266, 489, 544-545, 547-548

- meters for 230, 235, 237-239, 348
- three-stator 238
- two-stator 234, 237

phase shifting transformer for 233

VARs 23, 31-33, 73, 75, 188-189, 193, 210, 220, 222-223, 225, 229-230, 232, 239-247, 251, 257, 260-262, 264, 266, 339, 348, 489, 544, 546, 548

- definition 23
- measurement of 226, 244

Vector, *See* Phasor

Volt 23, 56, 73, 77, 270-271, 299, 489, 543, 545

- definition 23
- measurement of 103, 110-112, 118

Voltampere 24, 221, 223-225, 229-242, 265, 339, 341

- definition 24

Voltamperehour 235-236, 239

Voltmeter 27, 32, 43, 103-104, 109, 112-119, 124, 235, 264, 363-364, 366, 368, 370, 373, 455-456, 459, 468, 478, 562

## W

Water heater loads 283-285, 287

- measuring of 283-285

Watt 24, 133, 138-139, 143, 145, 148, 178-180, 184, 204-205, 207, 220, 243, 247, 254, 259-261, 264, 266, 287, 545

- definition 24
- standard of 544-545

Watthour 24, 32, 40-41

- definition 24
- standard of 541-542, 547, 550, 554

Watthour constant 42-43, 130, 157, 169, 254, 275, 279, 492, 501-502, 522, 524, 525

Watthour constant, primary 43, 275, 525

Watthour meter 127

- installation of 474-480, *See also* Service multi-stator 129-178
  - adjustments 157-160, 176
  - interdependence of 177
  - torque-balance 176-177
- Blondel's Theorem application to 131-132
- characteristics of 167, 172
- compensation in 161-166
- damping in 173
- damping torques in 172-173
- driving torques in 172-173
- four-wire, three-phase delta service 145-148
  - three-stator, use of 145-146
  - two-stator, three-current coil meter use of 146-148
- four-wire, three-phase Wye service, use on 138-139

- three-stator meter, use of
  - 138-139
- two-stator meter with three-current transformers 143-144
- two-stator, three-current coil meter, use of 139-143
- instrument transformers with
  - 148-150
- interference between stators
  - 174-175
- three-wire, three-phase delta service, use on 134-138
- single-stator 151-157
  - adjustments 157-160
    - full-load 158
    - inductive load 159-160
    - light-load 158
  - bearings in 168-169,
    - See also* Bearings
  - compensations in 161-166
    - overload for 161-163
    - temperature for 165-166
    - voltage for 164
  - frequency characteristics of 167
  - mechanical construction of 170-171
  - motor in 151-157
  - permanent magnets in 157
  - registers for 168
  - theory of torque production 172-173
  - two- or three-wire type 171
  - waveform, effect of on 167-168
- special 178
  - universal meters 178
- Wattour meter, maintenance of 523-526
  - bearings in 523
  - creeping, causes of 523
  - defective current and voltage coils in 526
  - friction, causes of 523
  - registers in 524
    - checking of 524-526
    - testing of 524-526
- Wattour meter, reading of, *See* Meter, reading of
- Wattour meter registers, *See* Register, wattour meter
- Wattour meter, testing of 487-527
  - basic, single-stator 500-502
    - adjustments for 503-506
      - full-load 503
      - lag 503-504
      - light-load 503
  - loading methods for 492-496
    - customer's 493
    - phantom 493-495
    - resistance 496
  - mobile shop, field 521-522
  - multi-stator 504-506
    - circuits for 506
    - photoelectric counters 506-507
    - rotary stepping switches 507
    - timing and speed measurements 506
  - on customer's premises 514-527
    - instrument transformers with 519
    - multi-stator field test procedure 518-519
    - network meters 521
    - preliminary procedures 515-516
    - relations with customers 514-515
    - safety precautions 515
    - single-stator field test procedures 516-518
    - three-phase, four-wire delta 521
    - three-phase, four-wire wye 521
    - three-stator 521
    - two-stator 521
  - reference standard for 488
  - shop 510-514
    - calibrating constants for 513-514
    - multi-stator meters 512-513
    - procedure variations 510
    - single-stator meters 510-512
  - test fixtures 507-510
    - gang boards 527
- Wattour, constant 9
  - definition 9
  - equation of 169
  - use, in present registration
    - calculations 40-44
      - in testing wattour meter registers 524
    - in testing wattour meters 500-502, 510-514
- Waveform 60-62, 77, 104-105, 108-110, 122, 128, 153-154, 167-168, 183-184, 186-187, 219, 221, 223, 246, 296-298, 307-308, 310, 364, 381, 394-395, 489, 495-497, 522, 545-546, 548-549, 555, 569
- Waves, sine 60, 168, 220, 387, 555
- Wheatstone bridge 8
  - definition 8
  - Wye circuits, *See* Polyphase, Wye connections